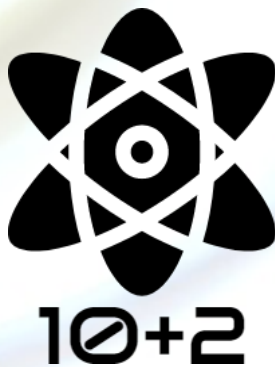


10+2 PCM NOTES

BY

JOYOSHISH SAHA

(PDF version handwritten notes of Maths, Physics and Chemistry for 10+2 competitive exams like JEE Main, WBJEE, NEST, IISER Entrance Exam, CUCET, AIPMT, JIPMER, EAMCET etc.)



Downloaded from <https://plustwopcm.blogspot.in/>
Visit the blog to get helpful notes for your 10+2 preparation.


With best wishes from Joyoshish Saha

* Growth & Decay of current in a LR circuit:

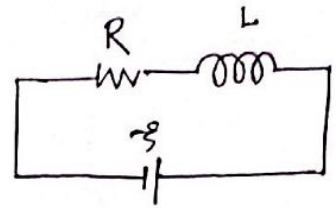i) Growth of current:

$$i = \frac{\mathcal{E}}{R} (1 - e^{-Rt/L})$$

$$i = i_0 (1 - e^{-t/\tau}) \quad \left[i_0 = \frac{\mathcal{E}}{R}, \tau = \frac{L}{R} \right]$$




At $t = \tau$, $i = 0.63 i_0$.

Time constant

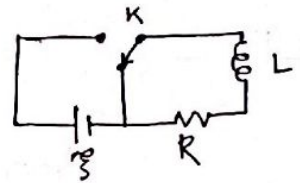ii) Decay of current:

$$i = i_0 e^{-\frac{R}{L}t} = i_0 e^{-t/\tau}$$




At $t = \tau$, $i = 0.37 i_0$.

* Charging & Discharging of Capacitor:

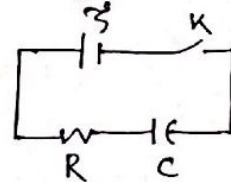i) Charging:

$$q = \mathcal{E}C (1 - e^{-\frac{t}{RC}})$$



$$q = \mathcal{E}C (1 - e^{-t/\tau}) \quad [\tau = RC] \quad \tau \rightarrow \text{Time cons.}$$

$$q = q_0 (1 - e^{-t/\tau}) \quad [q_0 = \mathcal{E}C]$$

At $t = \tau$, $q = 0.63 q_0$.

$$i = \frac{\mathcal{E}}{R} e^{-\frac{t}{RC}} = i_0 e^{-t/\tau}$$


At $t = \tau$, $i = 0.37 i_0$.

ii) Discharging:

$$q = q_0 e^{-t/\tau}$$


$$[q_0 = C\mathcal{E}, \tau = RC]$$
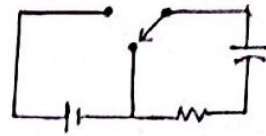
$$i = i_0 e^{-t/\tau} \quad [i_0 = \frac{q_0}{CR} = \frac{\mathcal{E}}{R}]$$



* Pure R circuit with AC:
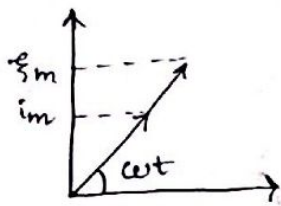
$$\mathcal{E} = \mathcal{E}_m \sin \omega t, \quad i = i_m \sin \omega t \quad [i_m = \frac{\mathcal{E}_m}{R}]$$




$$\begin{aligned} \bar{P} &= \frac{1}{2} i_m^2 R = i^2 R = iV \quad [i = \frac{i_m}{\sqrt{2}} \rightarrow \text{rms current}] \\ &= \frac{\mathcal{E}_m}{\sqrt{2}} \cdot \frac{i_m}{\sqrt{2}} \quad [V = \frac{\mathcal{E}_m}{\sqrt{2}} \rightarrow \text{rms voltage}] \end{aligned}$$

Impedance, $Z = R$

* Pure L circuit with AC:
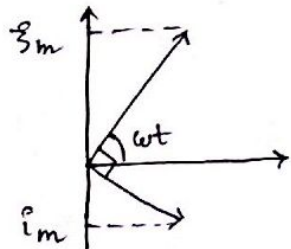
$$\mathcal{E} = \mathcal{E}_m \sin \omega t, \quad i = \frac{\mathcal{E}_m}{\omega L} \sin(\omega t - \frac{\pi}{2}) = i_m \sin(\omega t - \frac{\pi}{2})$$




$$\bar{P}_L = 0 \quad [\text{Wattless current}]$$

$$[i_m = \frac{\mathcal{E}_m}{\omega L}]$$

$$Z = \omega L \quad [i_m = \frac{\mathcal{E}_m}{Z}]$$

* Pure C circuit with AC:
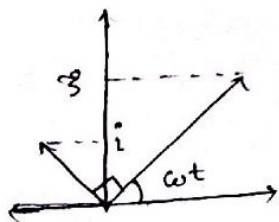
$$\mathcal{E} = \mathcal{E}_m \sin \omega t, \quad i = \mathcal{E}_m \omega C \sin(\omega t + \frac{\pi}{2}) = \frac{\mathcal{E}_m}{1/\omega C} \sin(\omega t + \frac{\pi}{2})$$




$$i = \frac{\mathcal{E}_m}{Z} \sin(\omega t + \frac{\pi}{2}) = i_m \sin(\omega t + \frac{\pi}{2})$$

$$\bar{P}_C = 0 \quad [\text{Wattless}]$$

$$Z = \frac{1}{\omega C}$$

* LCR series circuit with AC:
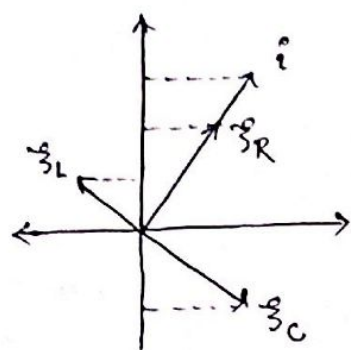
$$\mathcal{E} = \mathcal{E}_m \sin \omega t$$



$$i = \frac{\mathcal{E}_m}{\sqrt{R^2 + \left(\frac{1}{\omega C} - \omega L\right)^2}} \sin(\omega t - \phi)$$


$$= \frac{\mathcal{E}_m}{Z} \sin(\omega t - \phi)$$

$$\tan \phi = \frac{X_C - X_L}{R}$$

$$X_C = \frac{1}{\omega C}$$

$$X_L = \omega L$$
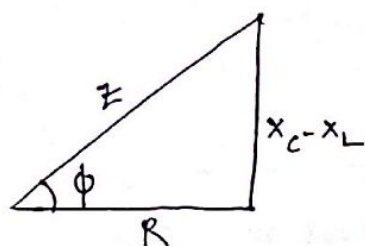
$$\frac{R}{Z} = \cos \phi, \quad \frac{X_C - X_L}{Z} = \sin \phi$$




$$P = \frac{1}{2} \frac{\mathcal{E}_m^2 R}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\Rightarrow P = P_m \frac{R^2}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

At half-maximum points, $P = \frac{1}{2} P_m$

$$P = \frac{1}{2} P_m \quad \left| \begin{array}{l} \omega_1 = \omega_0 - \Delta \omega \\ \omega_2 = \omega_0 + \Delta \omega \end{array} \right.$$
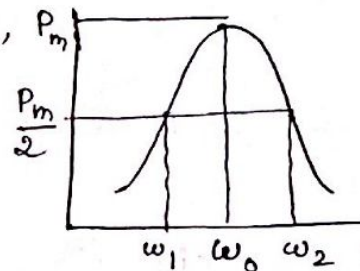
$$\& \quad 2\Delta \omega = \frac{R}{L}$$



Q-factor:

$$Q = \frac{\omega_0}{2\Delta \omega} = \frac{\omega_0 L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{\omega_0 C R}$$

Higher the value of Q , the sharper resonance occurs.

For resonance, $\omega_0 = \frac{1}{\sqrt{LC}}$. [$\omega_0 = 2\pi n$].

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

$\rightarrow i \rightarrow \text{maximum} \Rightarrow i = \frac{\mathcal{E}_m}{R}$

* Power in AC Circuit: The Power Factor:-

$$\bar{P} = i V \cos \phi = Z i^2 \cos \phi.$$

$\cos \phi$ is called the power factor.

* LC Oscillations: $\frac{d^2 q}{dt^2} + \frac{1}{LC} q = 0. \quad \left| \quad i = -\frac{dq}{dt} \right.$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \left| \quad \begin{aligned} q &= q_m \cos \omega_0 t \\ i &= \omega_0 q_m \sin \omega_0 t = i_m \sin \omega_0 t \\ (i_m &= \omega_0 q_m) \end{aligned} \right.$$

* LR Circuit: $q = q_m \sin \omega t.$

$$i = i_m \sin(\omega t - \theta) = \frac{q_m}{\sqrt{R^2 + (\omega L)^2}} \sin(\omega t - \theta).$$

$$\theta = \tan^{-1} \frac{\omega L}{R}.$$

$$\cos \theta = \frac{R}{\sqrt{R^2 + (\omega L)^2}}$$

$$\bar{P} = i V \cos \theta. \quad \left[V = \frac{q_m}{\sqrt{2}}, \quad i = \frac{i_m}{\sqrt{2}} \right].$$

* CR circuit:

$$i = i_0 \sin(\omega t + \theta) = \frac{q_m}{\sqrt{R^2 + \frac{1}{(\omega C)^2}}} \sin(\omega t + \theta).$$

$$\theta = \tan^{-1} \left(\frac{1}{C \omega R} \right).$$

$$\cos \theta = \frac{R}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}.$$

$$\bar{P} = i V \cos \theta.$$